

# Basic Electronics


## Chapter 2, 3A (test T5, T6) Basic Electrical Principles and the Functions of Components

Figures in this course book are reproduced with the permission of the American Radio Relay League.

This booklet was compiled by  
John P. Cross AB5OX

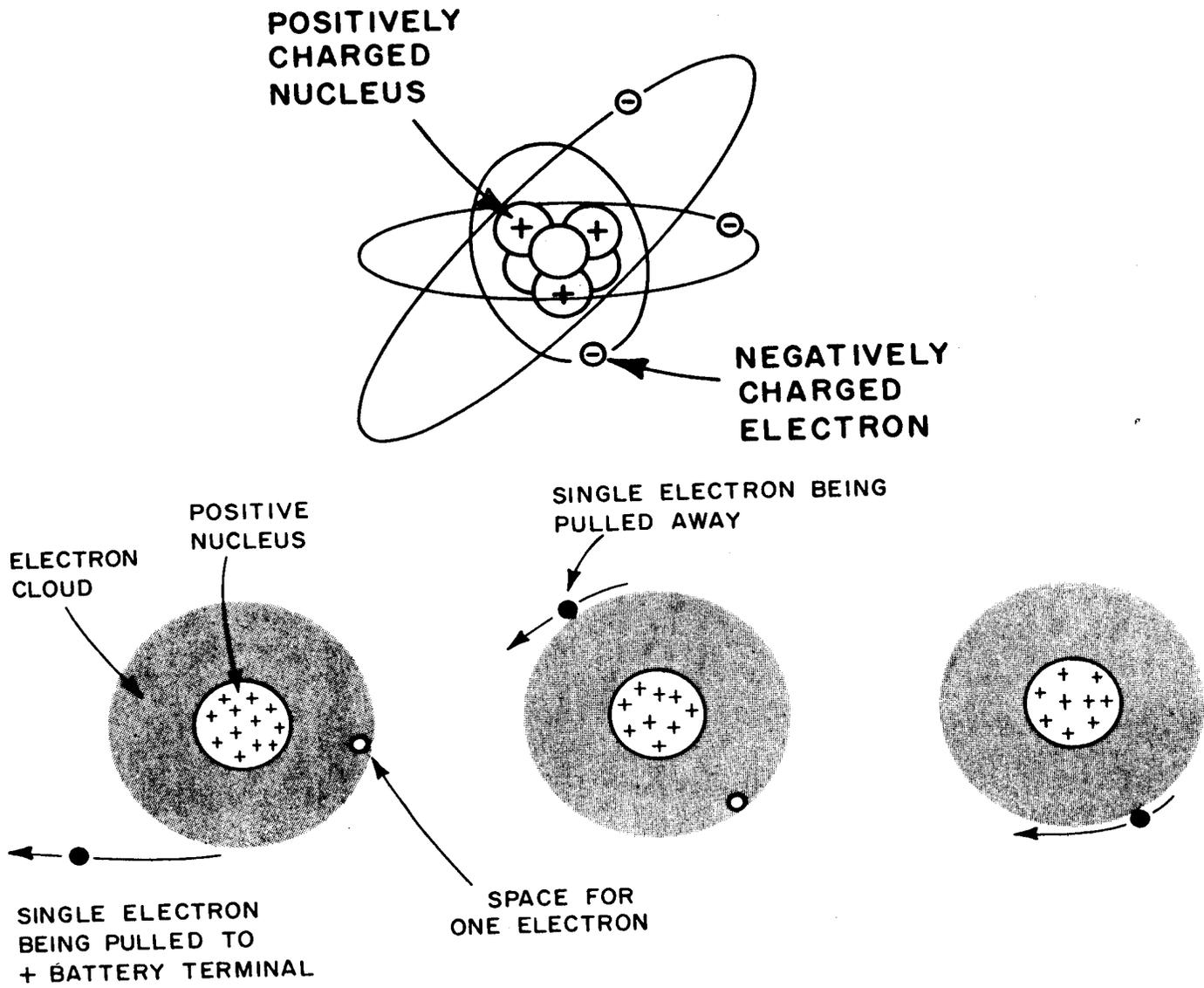
# Basic Electrical Principles

- Conductors - keep loose grip on their electrons and allow electrons to move freely. Metals are usually good conductors.
- Insulators - keep close hold of their electrons and do not allow free movement of electrons. Glass, wood, plastic, mica, fiberglass and air are good insulators.
- Electromotive Force (EMF) is the force that moves electrons through conductors. Its unit of measure is the Volt. Think of it as similar to a pressure.
- Voltage Source - has two terminals (+ and -). Some examples are car batteries (12 volts DC), D cell batteries (1.5 volts DC) and a wall socket (120 volts AC).
- Current - is the flow of electrons. It is measured in amperes. (convention - current sign is - to electron velocity)
- Resistance (ohms,  $\Omega$ ) is the ability to oppose an electrical current.




# Circuit Definitions


A circuit must close to be complete!

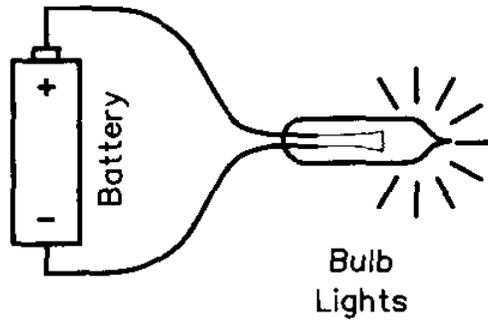

(A)

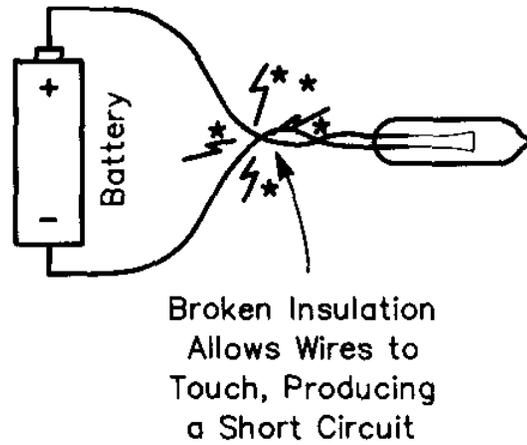


(B)


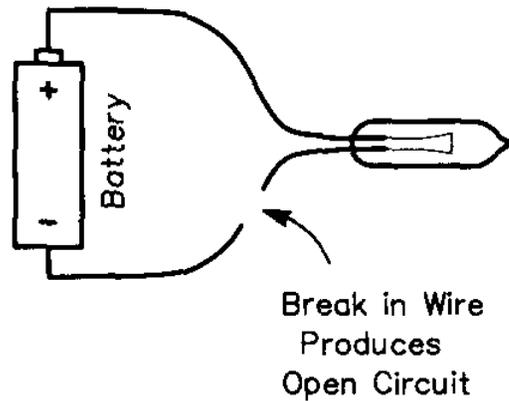


(C)
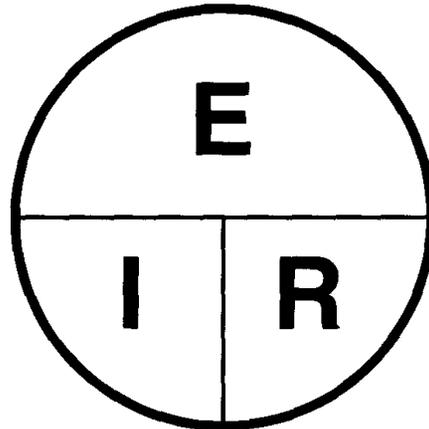
# Ohm's Law

- Ohm's Law relates Current (I), Voltage (E) and Resistance (R)
- The relationship can be written three ways:
  - »  $E = I \times R$
  - »  $I = E / R$
  - »  $R = E / I$



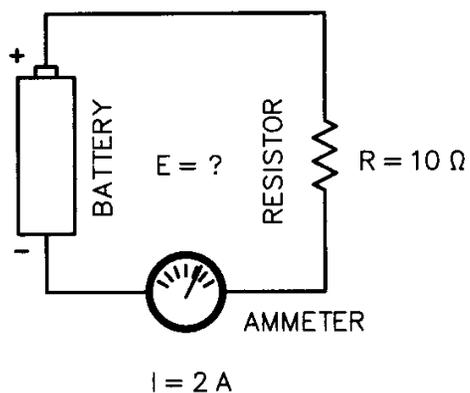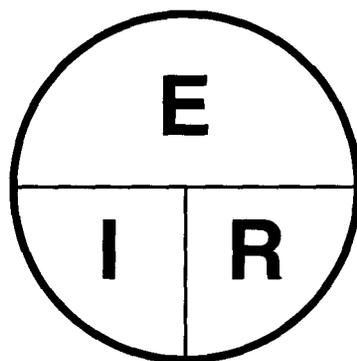


GIVEN:  $I = 2$  AMPERES  
 $R = 10$  OHMS

FIND:  $E$  (VOLTAGE)

$$E = I \times R = 2 \times 10 = 20$$

VOLTAGE EQUALS 20 VOLTS

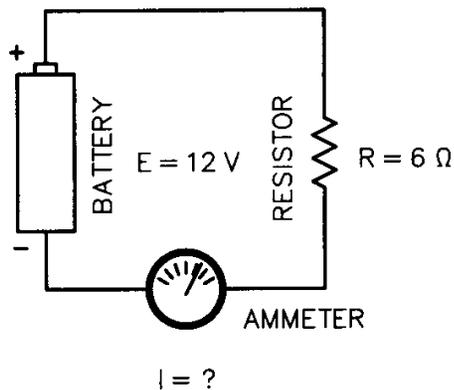


GIVEN:  $E = 12$  VOLTS  
 $R = 6$  OHMS

FIND:  $I$  (CURRENT)

$$I = \frac{E}{R} = \frac{12}{6} = 2$$

CURRENT EQUALS  
 TWO AMPERES

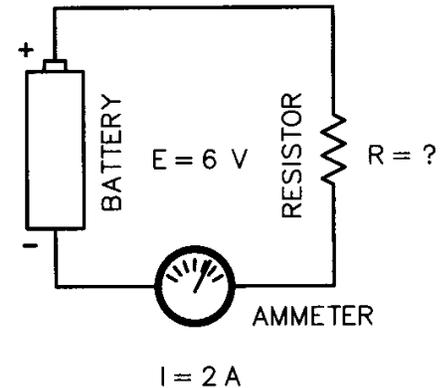

GIVEN:  $E = 6$  VOLTS  
 $I = 2$  AMPERES

FIND:  $R$  (RESISTANCE)

$$R = \frac{E}{I} = \frac{6}{2} = 3$$

RESISTANCE EQUALS  
 THREE OHMS

Figure 5-8—This drawing shows some Ohm's Law problems and solutions.

# Resistors



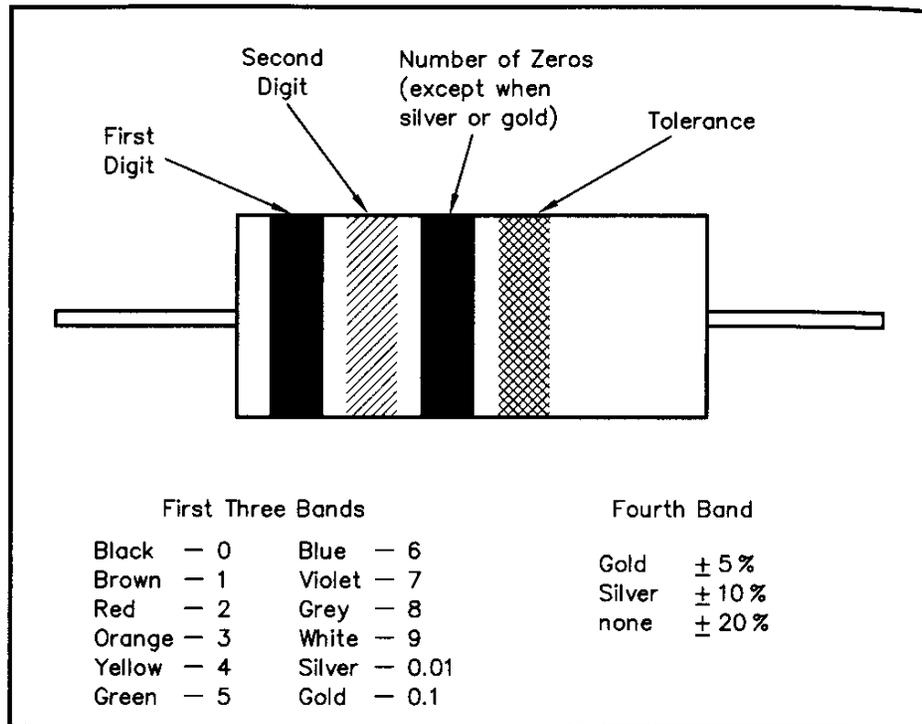
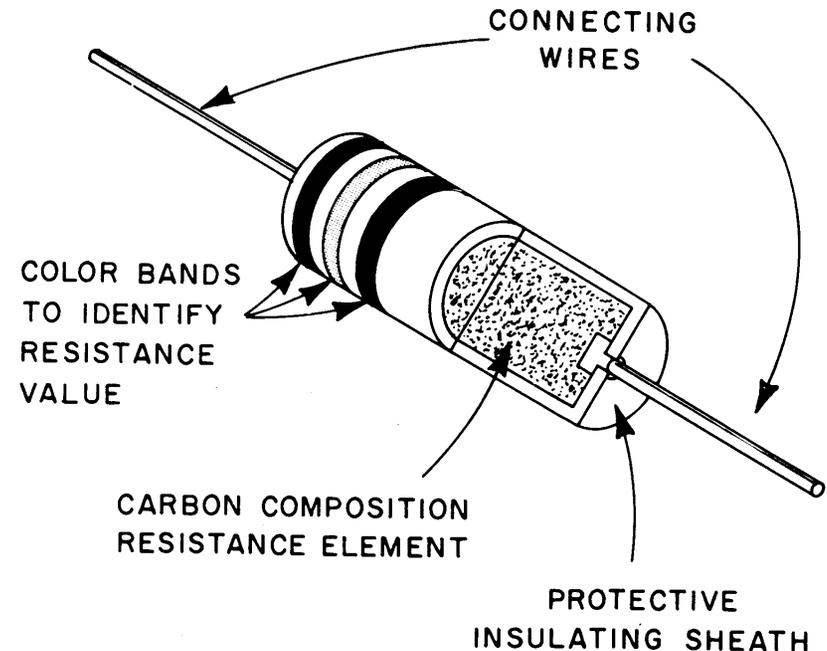


Figure 6-23 — Small resistors are labeled with a color code to show their value. For example, proceeding from left to right, a resistor with color bands of yellow/violet/brown/gold is a 470-Ω resistor with a 5% tolerance.


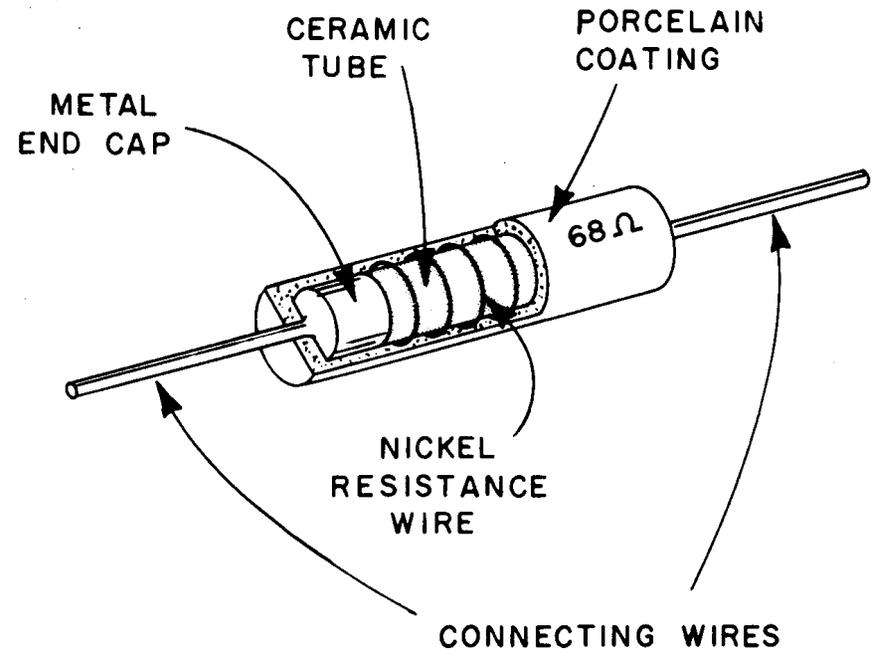
Mnemonic: “Black Bears Run On Young Grass By Violets Growing Wild”



# Resistor Types - Precision

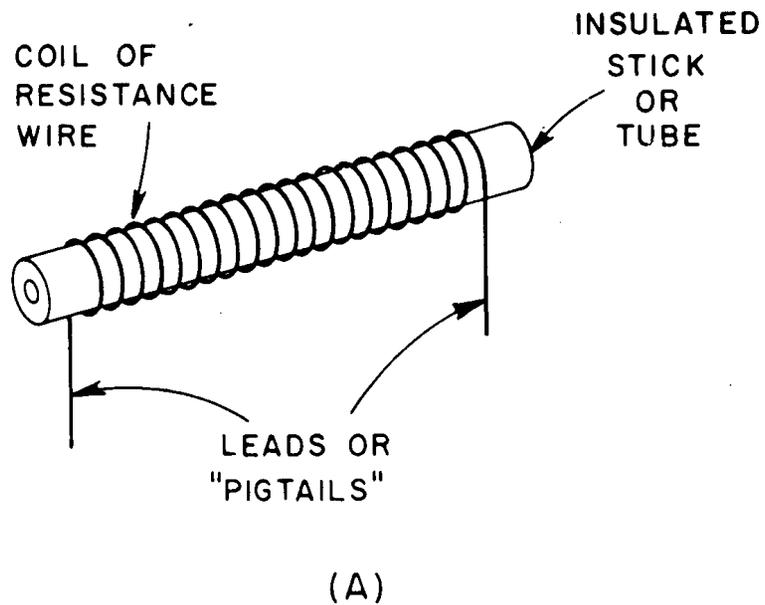


# Resistors - Film Type

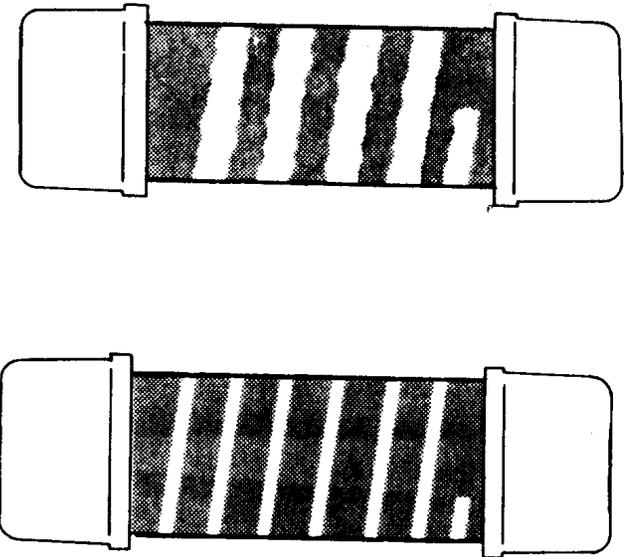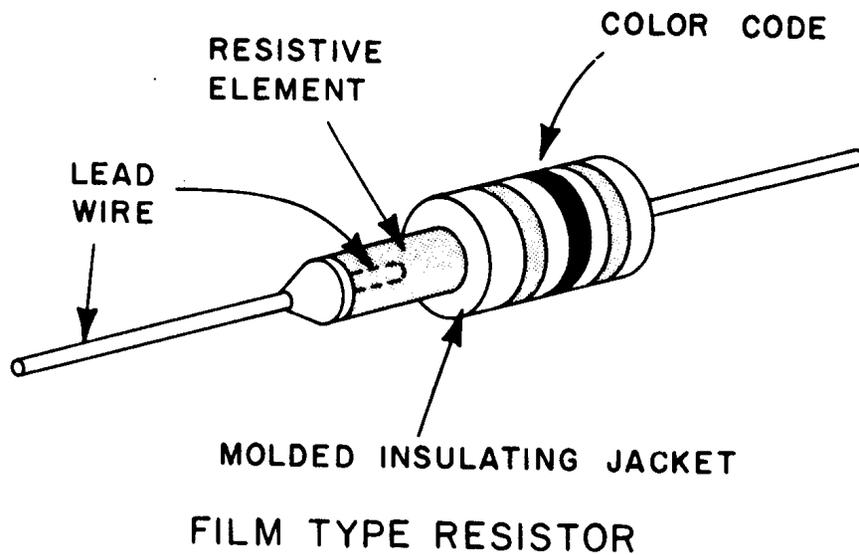


# Resistors - Variable
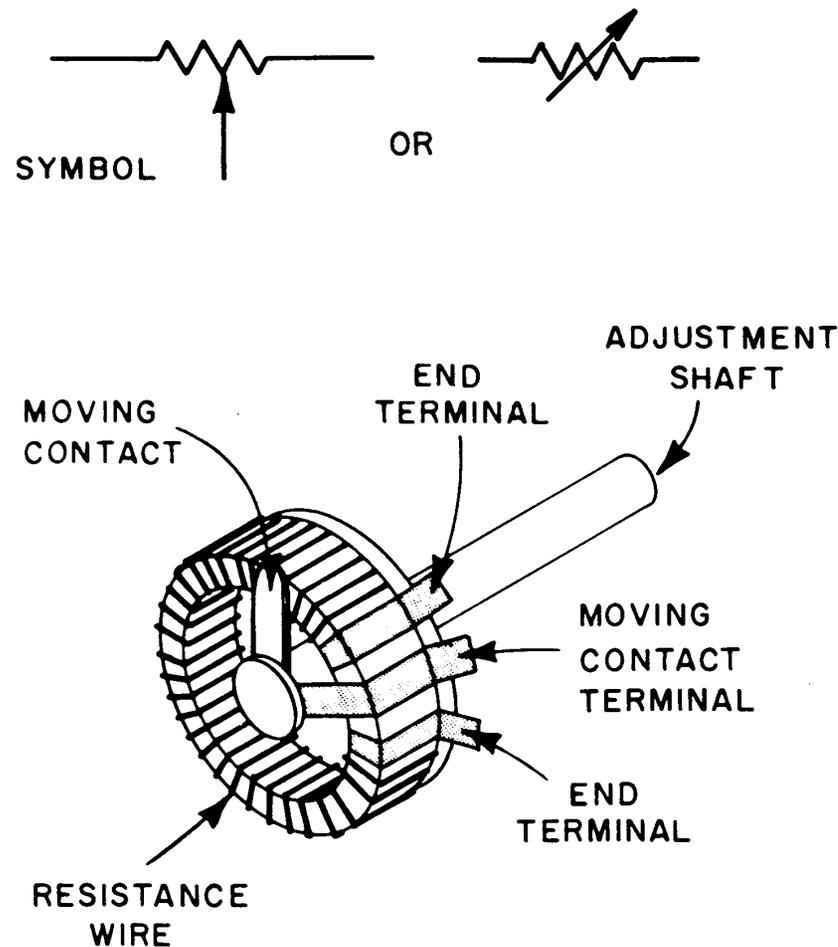
## Potentiometers used for volume control




# Calculating Resistance

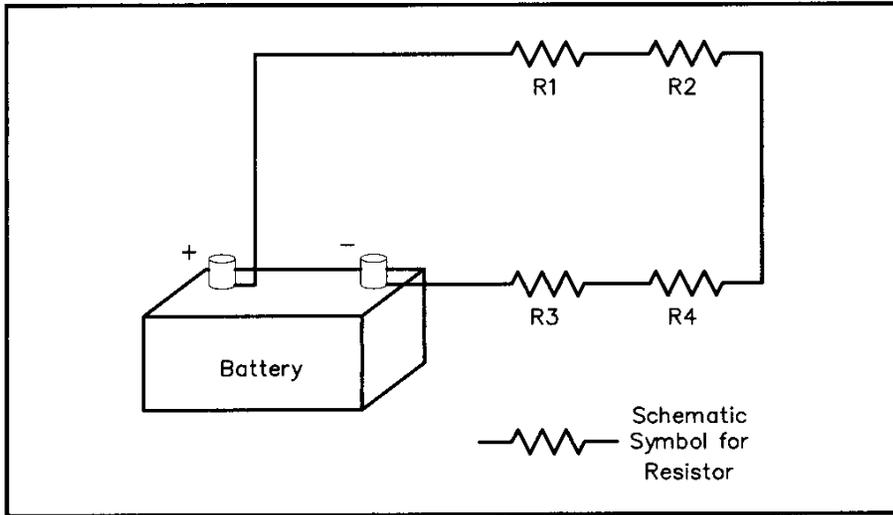

- Series:

$$R=R1+R2+R3+R4$$

(the voltage adds up)

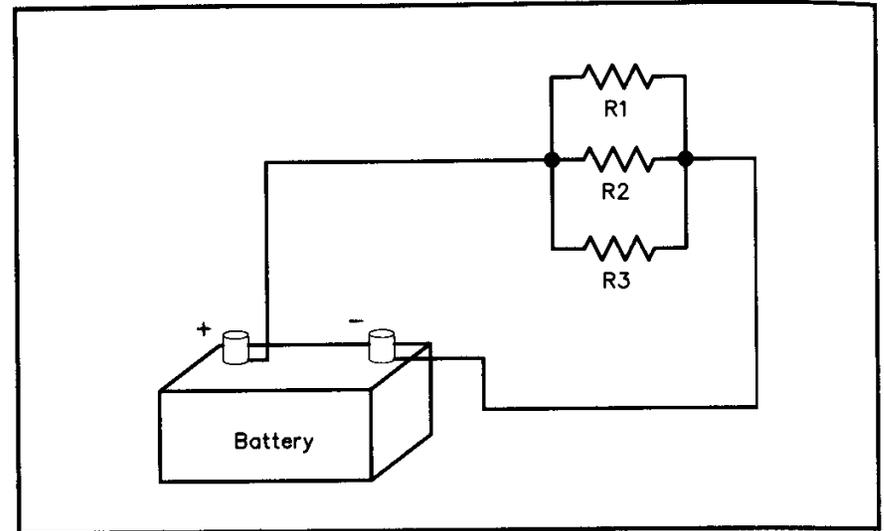

- Parallel:

$$1/R=1/R1+1/R2+1/R3$$


(the current adds up)

# Capacitors


- Capacitors store energy in an electric field
- Basic unit of capacitance is the farad (f)
- Series:  $1/C=1/C1+1/C2+1/C3$
- Parallel:  $C=C1+C2+C3$
- (opposite to resistance)
- Capacitance is determined by 3 factors:
  - » plate surface area
  - » plate spacing
  - » insulating material (dielectric)
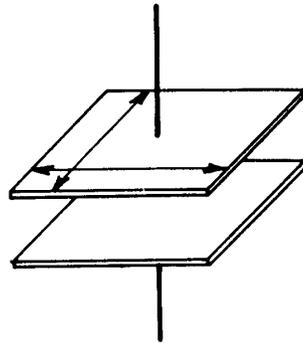
# Variables Determining Capacitance


CAPACITANCE  
VARIES  
DIRECTLY WITH  
PLATE SURFACE  
AREA



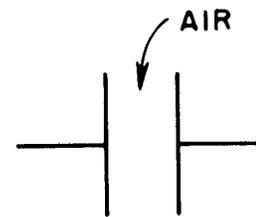CAPACITANCE VARIES WITH THE  
TYPE OF INSULATING MATERIAL USED




LOW  
CAPACITANCE

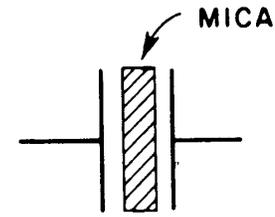


HIGH  
CAPACITANCE

DISTANCE  
BETWEEN  
PLATES

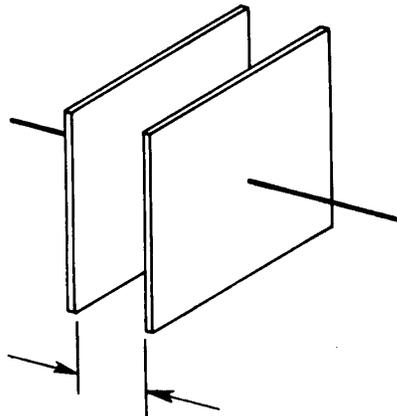


CAPACITANCE VARIES INVERSELY  
WITH THE DISTANCE BETWEEN  
PLATE SURFACES

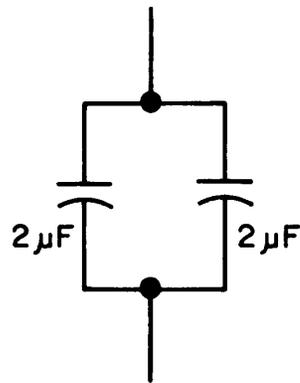
# Parallel Capacitors Increase Plate Area; increase charge so $C$



(A)

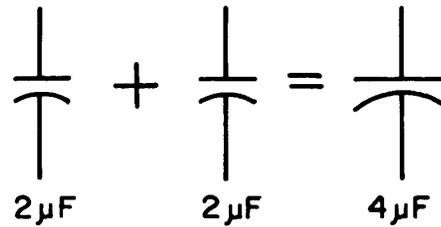

(B)

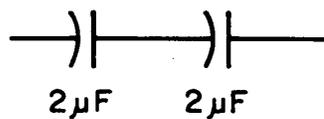


(C)





(D)

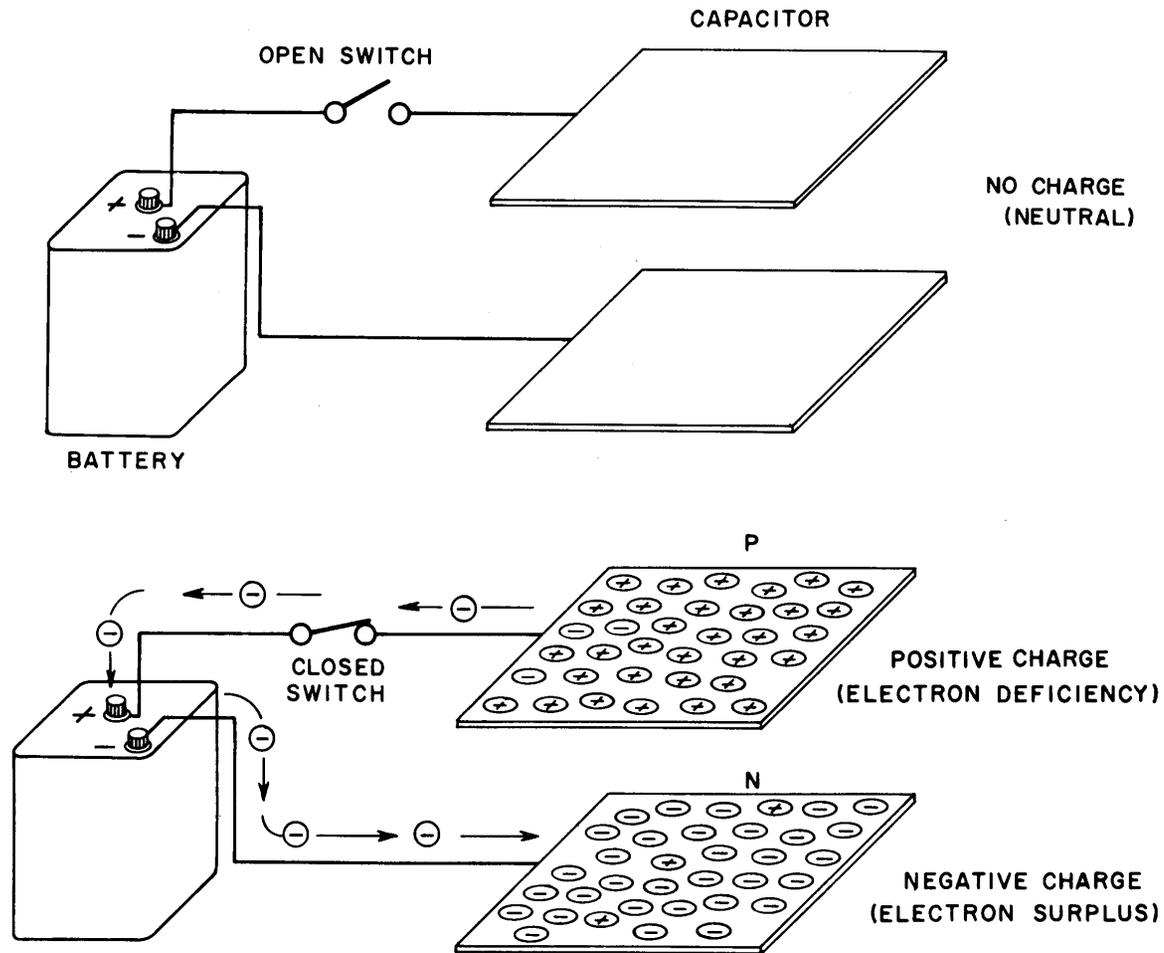
# Capacitors Store Energy in Electric Field



# Variable Capacitors

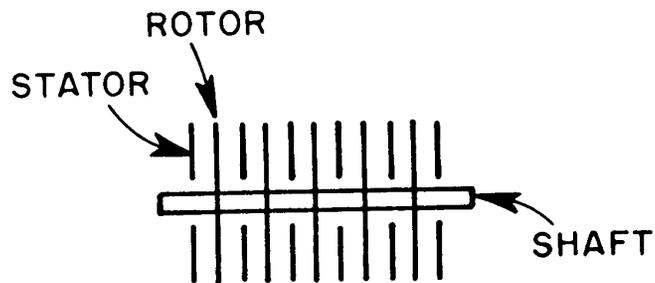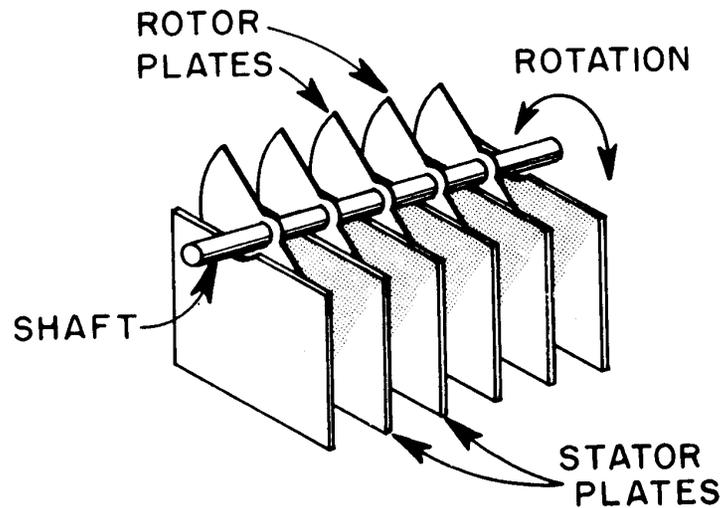

CROSS - SECTION  
**(A) AIR VARIABLE**

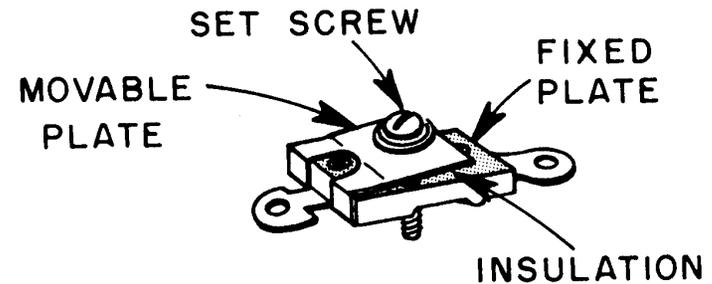


**(B) COMPRESSION TRIMMER**

# Inductors



- Inductors store energy in a magnetic field (like a little electromagnet)
- Basic unit of inductance is the henry (h)
- Parallel:  $1/L=1/L1+1/L2+1/L3$
- Series:  $L=L1+L2+L3$   
(like resistors)
- Inductance is determined by 4 factors:
  - » number of turns
  - » permeability of the core
  - » cross sectional area of the core
  - » spacing of the turns
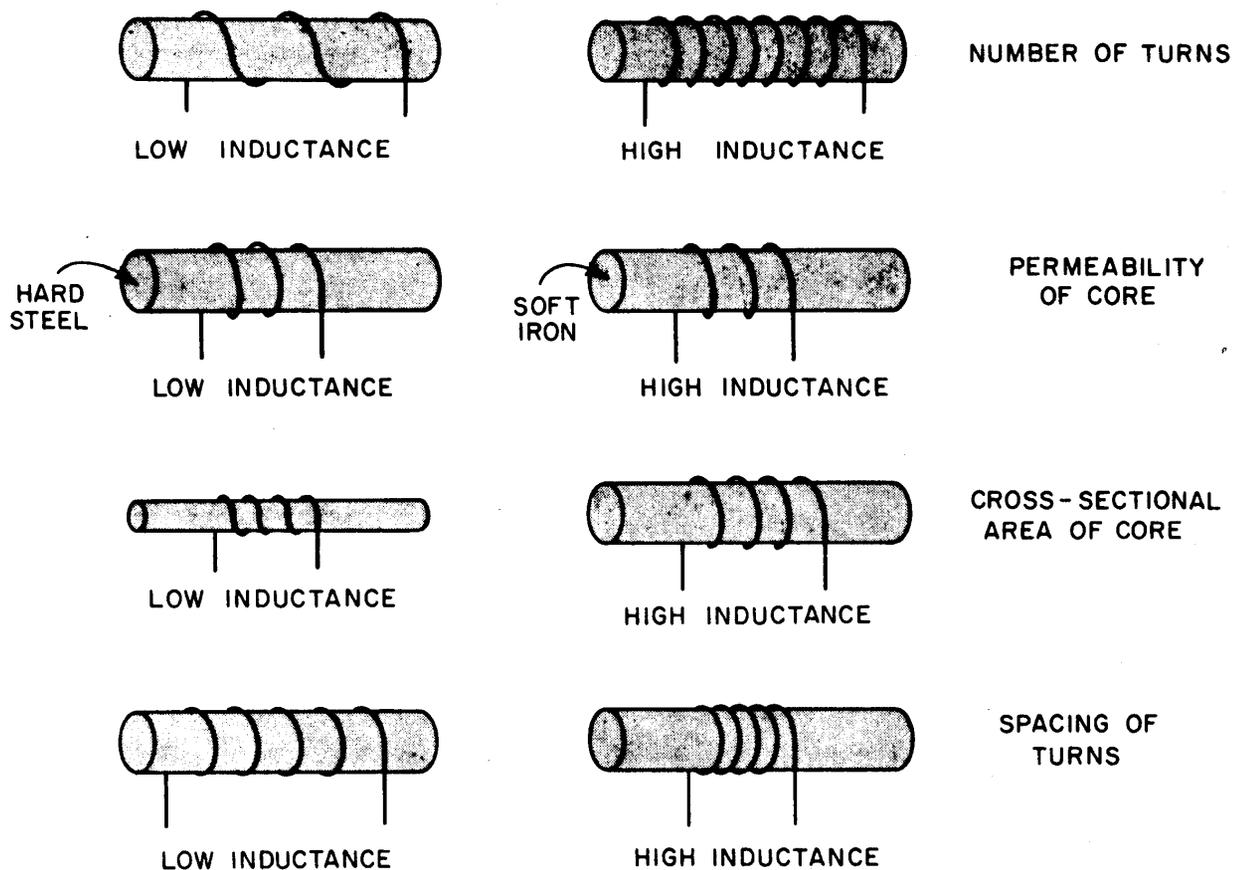
# Variables Determining Inductance

THE INDUCTANCE (L) OF A COIL DEPENDS ON....



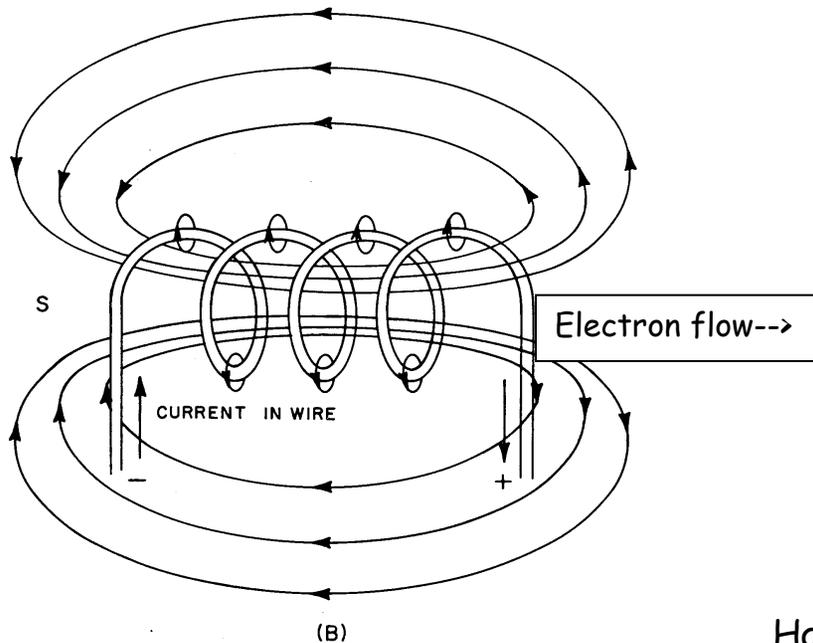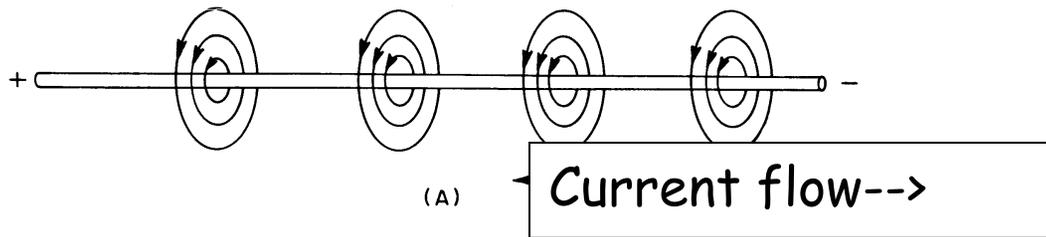
# Inductors Store Energy in Magnetic Field




Note: **current** flows from + to -, but is carried by **electrons** which flow from - to +


# Types of Inductors

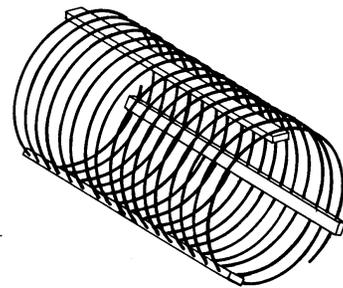


AIR-CORE

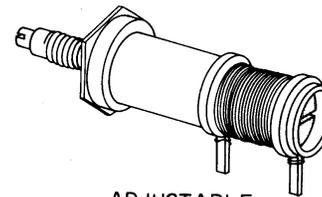

ADJUSTABLE

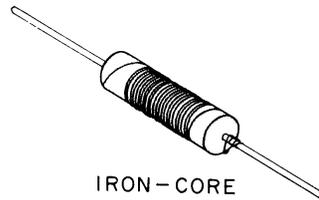

IRON-CORE

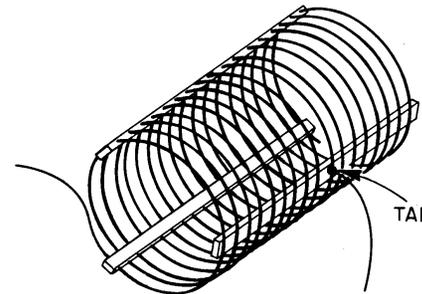

TAP




TAPPED

# Power

- Power is the rate of energy consumption.
- The basic unit of power is the watt (W)
- Power can be calculated as follows:
  - »  $P = I \times E$
- Since  $E = I \times R$ , you can also say:
  - »  $P = I^2 \times R$
- Since  $I = E / R$ , you can also say:
  - »  $P = E^2 / R$


# Meters - Measuring Current

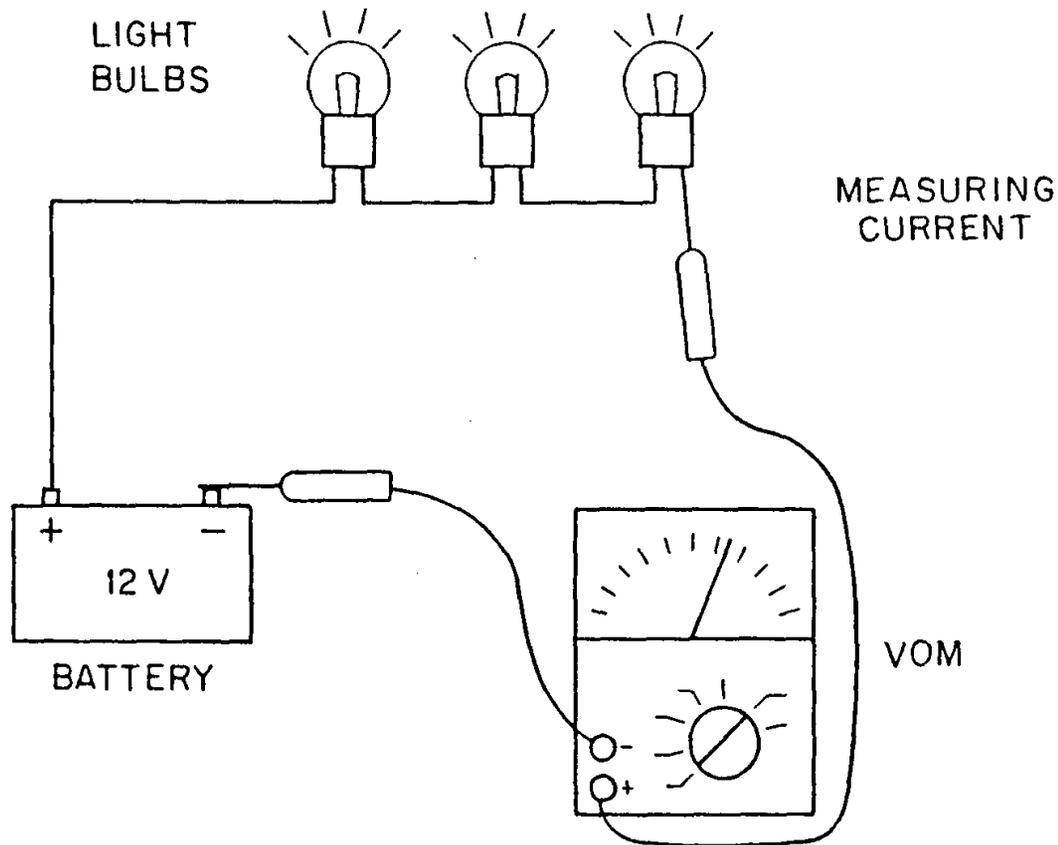

Ammeter  
must be  
part of the  
circuit to  
measure  
the current

VOM -  
multimeter  
that  
measures E,  
I, R

# Meters - Measuring Voltage

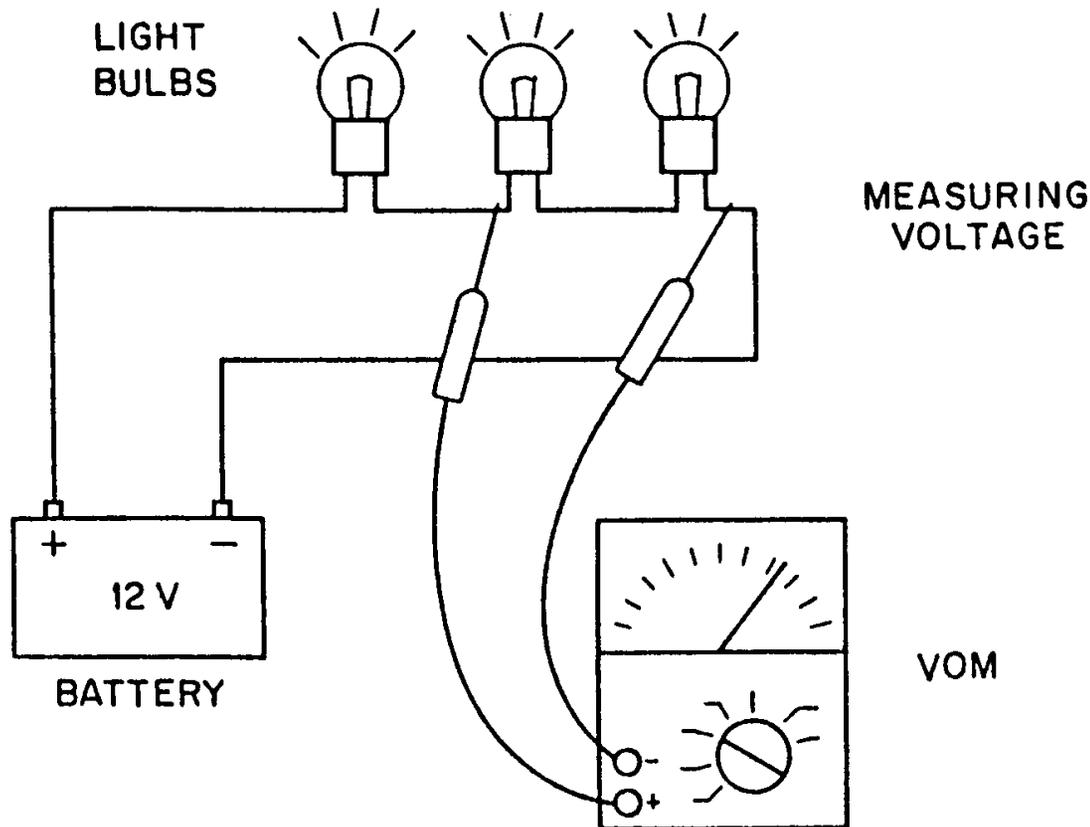

Voltmeter  
measures  
across the  
circuit (in  
parallel to  
the voltage  
to be  
measured)

# Meters - Measuring Resistance

Ohmmeter: measures **across** the resistor (but be sure the circuit is not turned on “hot”). Puts in a known voltage and measures the current, so it requires a battery. If the circuit is energized, will give the wrong reading!

Never leave a multimeter set at “ohms” - will run down its battery!

# Meters - Changing Range

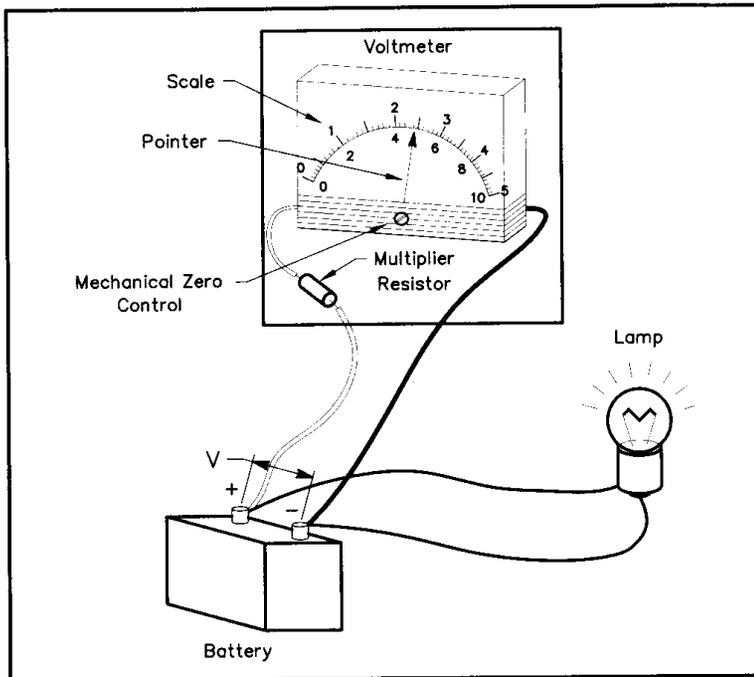


Figure 4-12—When you use a voltmeter to measure voltage, the meter must be connected in parallel with the voltage you want to measure.


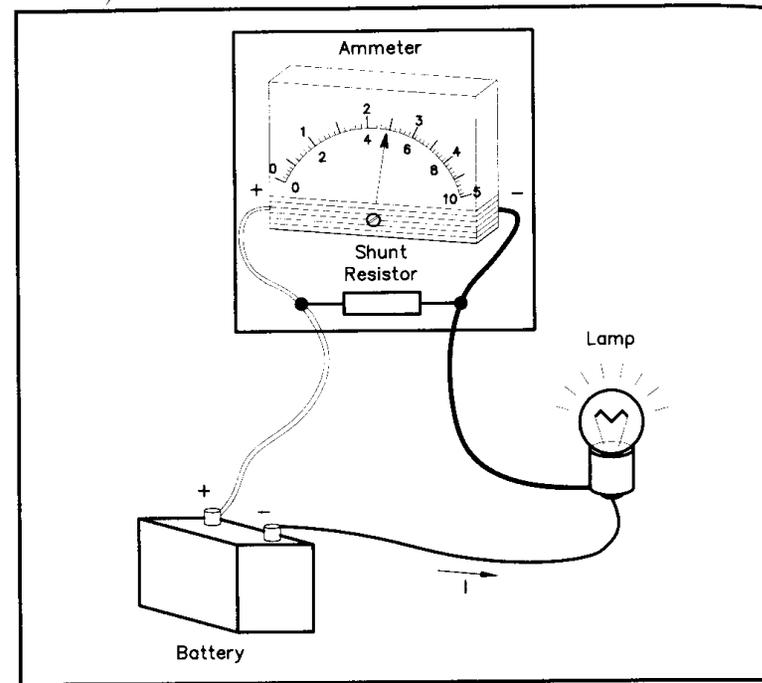


Figure 4-13—To measure current you must break the current at some point and connect the meter in series at the break. A shunt resistor expands the scale of the meter to measure higher currents than it could normally handle.

# Schematic Symbol Examples

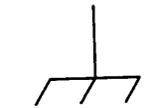

CHASSIS  
GROUND



EARTH  
GROUND




ANTENNA




VARIABLE  
RESISTOR



FIXED  
RESISTOR

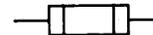


FUSE

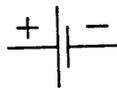


SINGLE-CELL  
BATTERY




MULTIPLE-CELL  
BATTERY

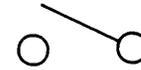


SINGLE-POLE,  
SINGLE-THROW  
SWITCH

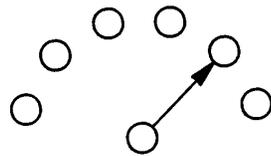

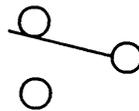SINGLE-POLE,  
6 POSITION  
ROTARY SWITCH




SINGLE-POLE,  
DOUBLE-THROW  
SWITCH

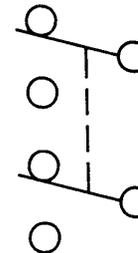


DOUBLE-POLE,  
DOUBLE-THROW  
SWITCH

# Schematic and Block Diagrams

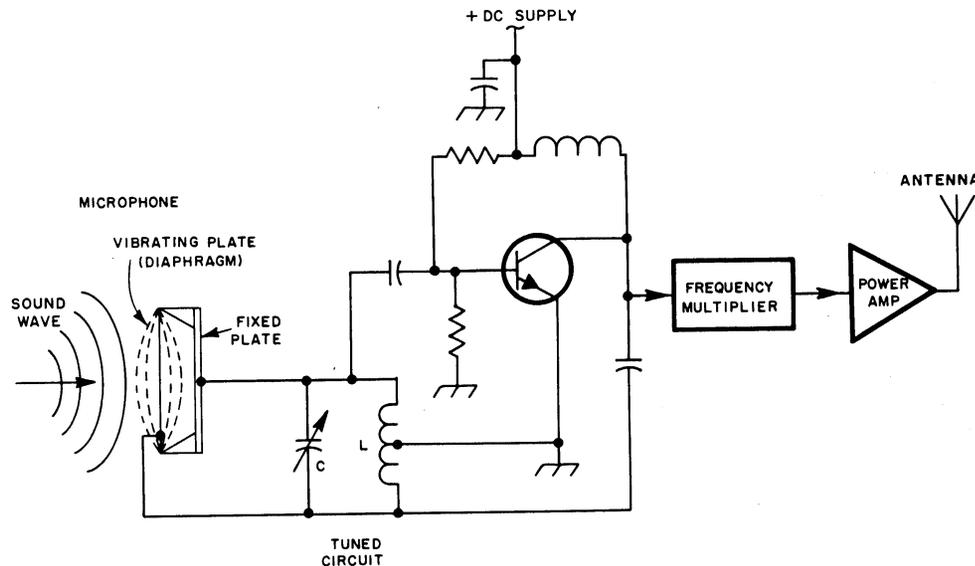

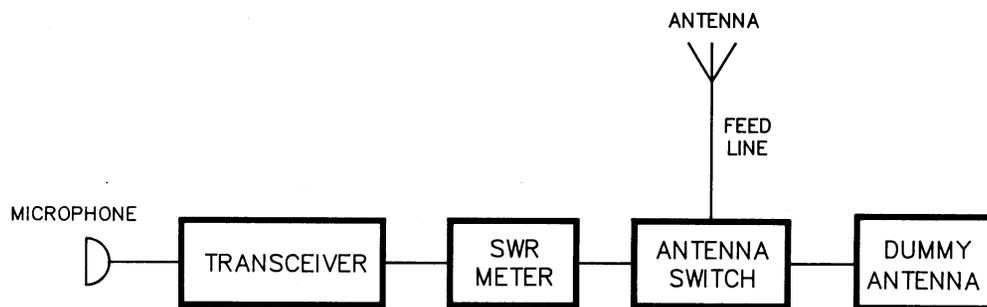- Schematic diagrams include all the individual components and how they are connected.



- Block diagrams show larger components (black boxes) and how they are connected

# International System of Units (SI)

## Metric Units

Prefix	Symbol	Multiplication Factor
exa	E	$10^{18}$ = 1,000,000,000,000,000,000
peta	P	$10^{15}$ = 1,000,000,000,000,000
tera	T	$10^{12}$ = 1,000,000,000,000
giga	G	$10^9$ = 1,000,000,000
mega	M	$10^6$ = 1,000,000
kilo	k	$10^3$ = 1,000
hecto	h	$10^2$ = 100
deca	da	$10^1$ = 10
(unit)		$10^0$ = 1
deci	d	$10^{-1}$ = 0.1
centi	c	$10^{-2}$ = 0.01
milli	m	$10^{-3}$ = 0.001
micro	$\mu$	$10^{-6}$ = 0.000001
nano	n	$10^{-9}$ = 0.000000001
pico	p	$10^{-12}$ = 0.000000000001
femto	f	$10^{-15}$ = 0.000000000000001
atto	a	$10^{-18}$ = 0.000000000000000001

# Metric Conversion Practice


Use these problems to practice converting between various units in the metric system. The following chart will help you decide which direction and how far to move the decimal point. Remember to move the decimal point to the right when the final unit you want is to the right of the beginning unit. Move the decimal point to the left when the final unit is to the left of the beginning unit. Count the number of places from the beginning unit to your final unit. That tells you how many places to move the decimal point.

G	M	K	h	da	UNIT	d	c	m	$\mu$	n	p
$10^9$	$10^6$	$10^3$	$10^2$	$10^1$	$10^0$	$10^{-1}$	$10^{-2}$	$10^{-3}$	$10^{-6}$	$10^{-9}$	$10^{-12}$


	Change	To
1)	1200 megahertz (MHz)	_____ gigahertz (GHz)
2)	7150 kilohertz (kHz)	_____ megahertz (MHz)
3)	1.4 gigahertz (GHz)	_____ megahertz (MHz)
4)	3.525 megahertz (MHz)	_____ kilohertz (kHz)
5)	3725 kilohertz (kHz)	_____ hertz (Hz)
6)	400 centimeters (cm)	_____ meters (m)
7)	3000 milliamperes (mA)	_____ amperes (A)
8)	3500 millivolts (mV)	_____ volts (V)
9)	500,000 microfarads ( $\mu$ F)	_____ farads (F)
10)	1,000,000 picofarads (pF)	_____ microfarads ( $\mu$ F)
11)	25,000,000 picofarads (pF)	_____ farads (F)
12)	25 microhenrys ( $\mu$ H)	_____ henrys (H)
13)	1270 megahertz (MHz)	_____ gigahertz (GHz)
14)	21.230 megahertz (MHz)	_____ kilohertz (kHz)
15)	28,300 kilohertz (kHz)	_____ megahertz (MHz)
16)	7.150 megahertz (MHz)	_____ kilohertz (kHz)
17)	3700 kilohertz (kHz)	_____ hertz (Hz)
18)	21,000,000 hertz (Hz)	_____ kilohertz (kHz)
19)	28,100,000 hertz (Hz)	_____ megahertz (MHz)
20)	7.100 megahertz (MHz)	_____ hertz (Hz)

- **Decibels** - logarithmic power scale  
(questions T5B09, 10, 11)
- 10 decibels = factor of ten in power
- =  $10 * \log ( \text{Power 2} / \text{Power 1} )$
- 3 dB is factor of 2
- 6 dB is 4 ( $2*2$ ); 9 dB is 8 ( $2*2*2$ )
- 5 dB is factor of pi (since  $\pi*\pi$  is almost 10)


# Amplifiers

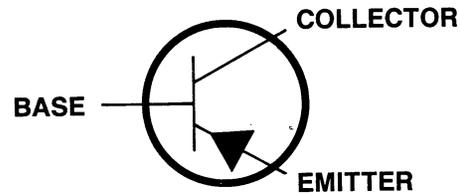

PNP  
TRANSISTOR

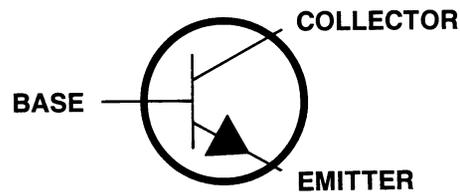

NPN  
TRANSISTOR

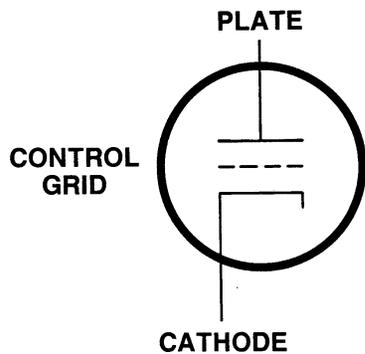


TRIODE  
VACUUM  
TUBE


- Tubes and transistors amplify signals applied to base or control grid. The amount of amplification is called **GAIN**.
- Transistors have advantages:
  - size
  - power consumption
  - cooling
  - robustness
- Tubes have advantages:
  - high power




# Amplifiers

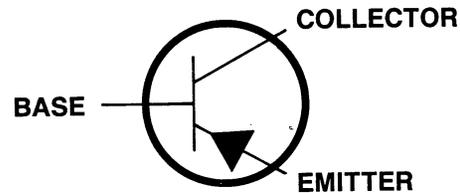

PNP  
TRANSISTOR

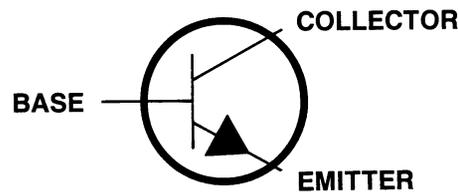

NPN  
TRANSISTOR

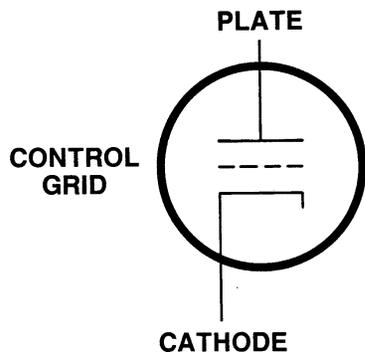


TRIODE  
VACUUM  
TUBE

- FET is Field Effect Transistor, and has a “gate” electrode.
- The component with an emitter electrode is a bipolar transistor.
- An integrated circuit is a device that combines several components into one package (generally including transistors)


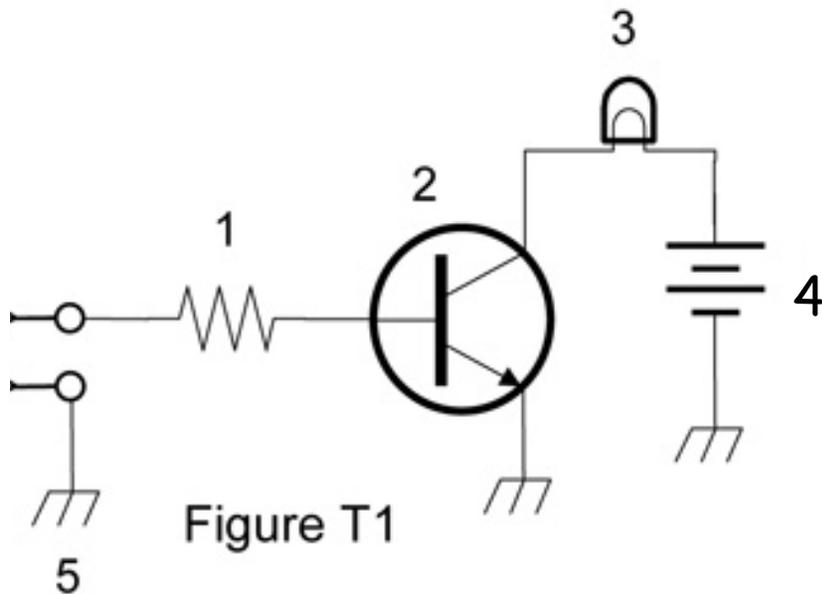
# Typical Circuit Diagrams

- 1 is a resistor
- 2 is a transistor (NPN)
- 3 is a lamp
- 4 is a battery
- 5 is chassis ground



# Typical Circuit Diagrams

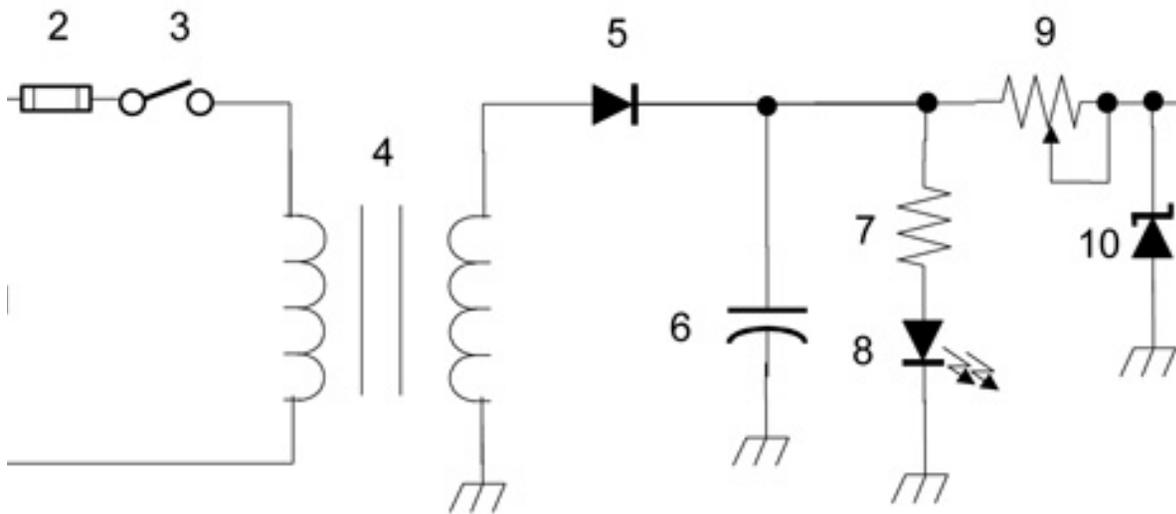


Figure T2

- 3 is a switch (single-pole, single throw)
- 4 is a transformer
- 5 is a diode
- 6 is a capacitor
- 7 is a resistor
- 8 is a light-emitting diode (LED)
- 9 is a variable resistor
- 10 is a diode

# Typical Circuit Diagrams

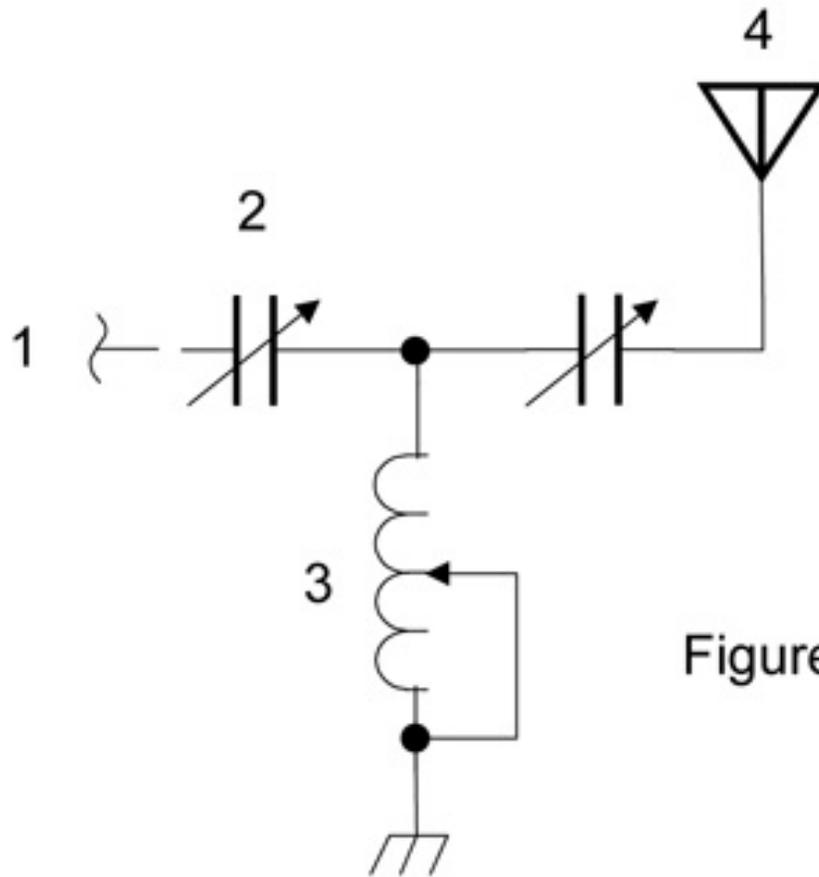


Figure T3

- 1 is an AC current
- 2 and 4 is a variable capacitor
- 3 is a variable inductor
- 4 is an antenna
- Note: diagrams do not represent true wire lengths

# Test Equipment

- Voltmeter - an instrument that is used to measure voltage.
  - It is used in parallel with a circuit to be measured.
  - a series resistor extends the range of the meter.
- Ammeter - an instrument used to measure amperage in a circuit.
  - It is hooked up in series with the circuit to be tested.
  - A shunt resistor (in parallel w/meter) extends the range of the meter.
- Multimeter - combines the functions above with resistance and others to make a versatile piece of test equipment.
- Wattmeter - a device that measures power coming from a transmitter through the antenna feed line. A directional wattmeter measures forward and reflected power. Wattmeters generally are useful in certain frequency ranges
- Signal Generator - a device that produces a stable, adjustable low level signal (AF or RF). It can be used to tune circuits.